

# CS1050-Computer organization and digital design

## Lab 7 – 7-Segment Display

Student Name: De Silva A.D.D.T.

Index Number: 220098C


Group Number: 33

### 1. Introduction
 
#### 1.1. Introduce the lab task

Main task of this lab is to design 7-Segment Display which is a simple electronic device that is used to display decimal numerals and some alphabetic characters. In this lab we designed a 7-segments display to display the output of our 4-bit arithmetic unit (developed in lab 6) as a hexadecimal number.

For that first we developed a lookup table using ROM. It was used to map the 4-bit sum to the 7-segments on the display. Finally, we verified the functionality of the circuit via simulation and on the development board.



(a picture of a 7-segment display)

#### 1.2. Table of segments to switch on

Output from RCA					Segment to switch on						
S3	S2	S1	S0	Hex. value	A	B	C	D	E	F	G
0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	1	0	0	1	1	1	1
0	0	1	0	2	0	0	1	0	0	1	0
0	0	1	1	3	0	0	0	0	1	1	0
0	1	0	0	4	1	0	0	1	1	0	0
0	1	0	1	5	0	1	0	0	1	0	0
0	1	1	0	6	0	1	0	0	0	0	0
0	1	1	1	7	0	0	0	1	1	1	1

1	0	0	0	8	0	0	0	0	0	0	0
1	0	0	1	9	0	0	0	0	1	0	0
1	0	1	0	A	0	0	0	1	0	0	0
1	0	1	1	B	1	1	0	0	0	0	0
1	1	0	0	C	0	1	1	0	0	0	1
1	1	0	1	D	1	0	0	0	0	1	0
1	1	1	0	E	0	1	1	0	0	0	0
1	1	1	1	F	0	1	1	1	0	0	0

## 2. Lookup Tables

### 2.1. Design source file

```

-----
-- Company:
-- Engineer:  DE SILVA A D D T
--
-- Create Date: 03/21/2024 02:35:11 PM
-- Design Name:
-- Module Name: LUT_16_7 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

signal sevenSegment_ROM : rom_type := (
    "1000000", --0
    "1111001", --1
    "0100100", --2
    "0110000", --3
    "0011001", --4
    "0010010", --5
    "0000010", --6
    "1111000", --7
    "0000000", --8
    "0010000", --9
    "0001000", --a
    "0000011", --b
    "1000110", --c
    "0100001", --d
    "0000110", --e
    "0001110"  --f );


begin

data <= sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;

```

## 2.2. Elaborated design schematic

 

## 2.3. Simulation source file

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 03/21/2024 03:11:06 PM  
-- Design Name:  
-- Module Name: LUT_16_7_Sim - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;
```

```
entity LUT_16_7_Sim is
-- Port ( );
end LUT_16_7_Sim;

architecture Behavioral of LUT_16_7_Sim is

component LUT_16_7
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

signal address : STD_LOGIC_VECTOR (3 downto 0);
signal data : STD_LOGIC_VECTOR (6 downto 0);

begin
    uut: LUT_16_7
        port map(
            address=>address,
            data=>data);

    process
    begin

        address<="0010";
        wait for 100ns;

        address<="0010";
        wait for 100ns;

        address<="0000";
        wait for 100ns;


        address<="0000";
        wait for 100ns;

        address<="1001";
        wait for 100ns;

        address<="1000";
        wait for 100ns;

        address<="1100";
        wait;
    end process;
end Behavioral;
```

## 2.4. Timing diagram

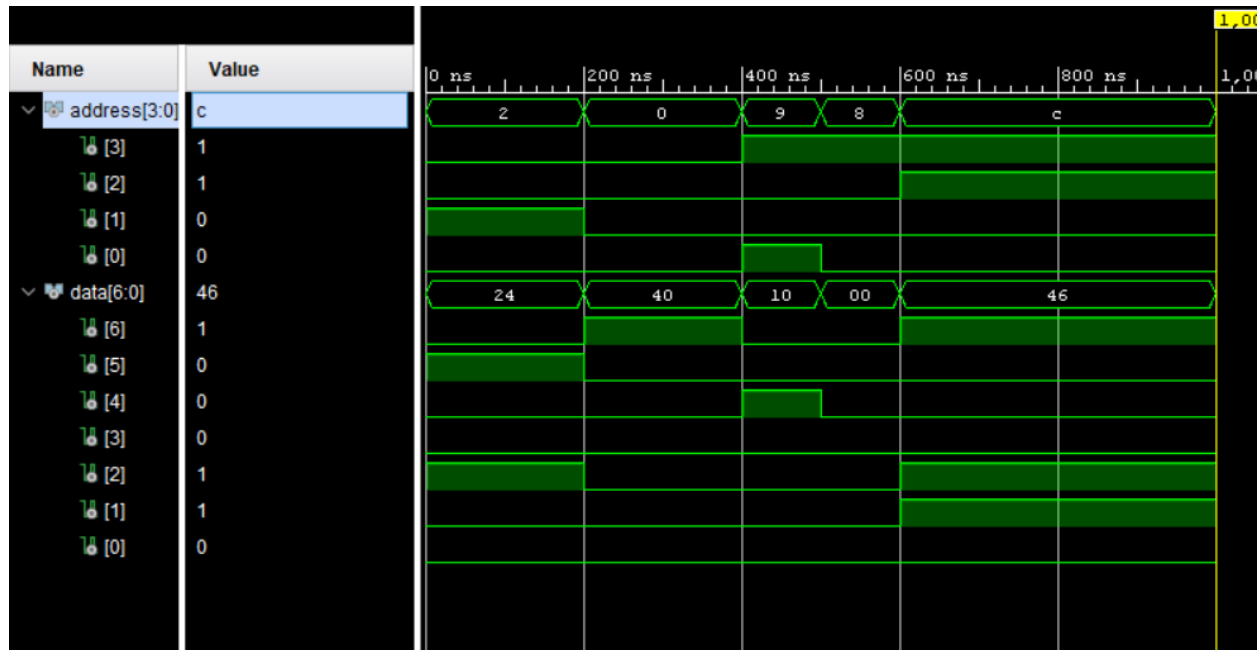

## 3. 7-Segment Display

### 3.1. Design source file

```
-----
-- Company:
-- Engineer: DE SILVA A D D T
--
-- Create Date: 03/21/2024 03:43:50 PM
-- Design Name:
-- Module Name: AU_7_seg - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
```

```

-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity AU_7_seg is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          Clk : in STD_LOGIC;
          RegSel : in STD_LOGIC;
          S_LED : out STD_LOGIC_VECTOR (3 downto 0);
          S_7Seg : out STD_LOGIC_VECTOR (6 downto 0);
          Carry : out STD_LOGIC;
          Zero : out STD_LOGIC);
end AU_7_seg;

architecture Behavioral of AU_7_seg is

component AU
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          RegSel : in STD_LOGIC;
          Clk : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          Zero : out STD_LOGIC;
          Carry : out STD_LOGIC);
end component;

component LUT_16_7
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

signal sum : std_logic_vector(3 downto 0);

```

```


begin
AU0: AU
  port map(
    A=>A,
    RegSel=>RegSel,
    Clk=>Clk,
    S=>sum,
    Zero=>Zero,
    Carry=>Carry);

LUT0: LUT_16_7
  port map(
    address=>sum,
    data=>S_7Seg);

S_LED<=sum;
end Behavioral;



```

### 3.2. Elaborated design schematic

 



### 3.3. Implemented design schematic

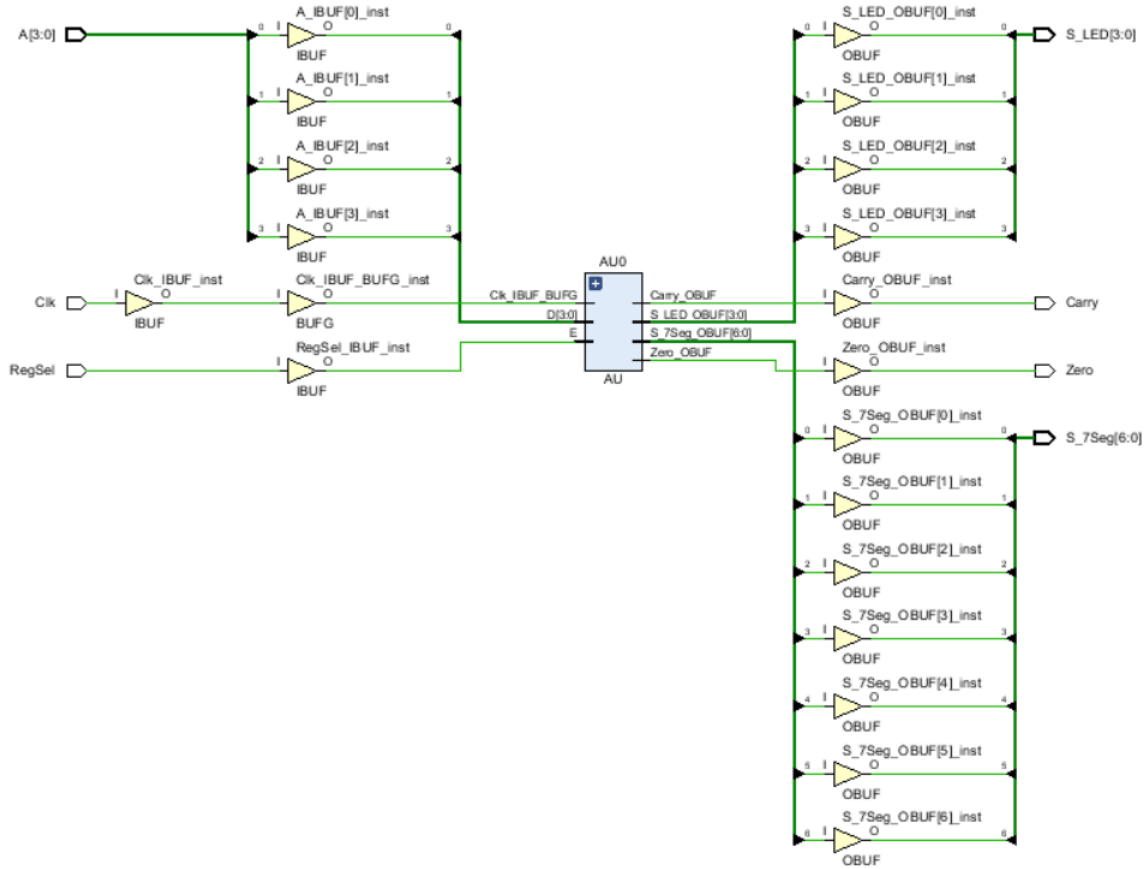 

### 3.4. Constraints file

```
1
2  ## Clock signal
3  set_property PACKAGE_PIN W5 [get_ports Clk]
4      set_property IOSTANDARD LVCMOS33 [get_ports Clk]
5      create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports Clk]
6
7  ## Switches
8  set_property PACKAGE_PIN V17 [get_ports {A[0]}]
9      set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]
10 set_property PACKAGE_PIN V16 [get_ports {A[1]}]
11     set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]
12 set_property PACKAGE_PIN W16 [get_ports {A[2]}]
13     set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]
14 set_property PACKAGE_PIN W17 [get_ports {A[3]}]
15     set_property IOSTANDARD LVCMOS33 [get_ports {A[3]}]
16
17 set_property PACKAGE_PIN R2 [get_ports {RegSel}]
18     set_property IOSTANDARD LVCMOS33 [get_ports {RegSel}]
19
20 ## LEDs
21 set_property PACKAGE_PIN U16 [get_ports {S_LED[0]}]
22     set_property IOSTANDARD LVCMOS33 [get_ports {S_LED[0]}]
23 set_property PACKAGE_PIN E19 [get_ports {S_LED[1]}]
24     set_property IOSTANDARD LVCMOS33 [get_ports {S_LED[1]}]
25 set_property PACKAGE_PIN U19 [get_ports {S_LED[2]}]
26     set_property IOSTANDARD LVCMOS33 [get_ports {S_LED[2]}]
27 set_property PACKAGE_PIN V19 [get_ports {S_LED[3]}]
28     set_property IOSTANDARD LVCMOS33 [get_ports {S_LED[3]}]
29
30 set_property PACKAGE_PIN P1 [get_ports {Carry}]
31     set_property IOSTANDARD LVCMOS33 [get_ports {Carry}]
32 set_property PACKAGE_PIN L1 [get_ports {Zero}]
33     set_property IOSTANDARD LVCMOS33 [get_ports {Zero}]
34
35
36 ##7 segment display
37 set_property PACKAGE_PIN W7 [get_ports {S_7Seg[0]}]
38     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[0]}]
39 set_property PACKAGE_PIN W6 [get_ports {S_7Seg[1]}]
40     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[1]}]
41 set_property PACKAGE_PIN U8 [get_ports {S_7Seg[2]}]
42     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[2]}]
43 set_property PACKAGE_PIN V8 [get_ports {S_7Seg[3]}]
44     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[3]}]
45 set_property PACKAGE_PIN U5 [get_ports {S_7Seg[4]}]
46     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[4]}]
47 set_property PACKAGE_PIN V5 [get_ports {S_7Seg[5]}]
48     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[5]}]
49 set_property PACKAGE_PIN U7 [get_ports {S_7Seg[6]}]
50     set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[6]}]
51
52
```

#### **4. Conclusion**

This lab focused on designing a 7-segment display interface for a 4-bit Arithmetic Unit. By utilizing a ROM-based lookup table, the 4-bit sum generated by the Arithmetic Unit was mapped to the appropriate segments for hexadecimal display. Through simulation, we gained practical insights into digital design, ROM usage, and circuit interfacing.