# CS1050-Computer organization and digital design

### Lab 5 - Counters

.....

Student Name: De Silva A.D.D.T.

Index Number: 220098C

Group Number: 33

### 1. Introduction

## Lab task

In this lab, we designed a 3-bit counter, a slowdown clock and a D flip-flop. The 3-bit counter was developed using slowdown clock and D flip-flop. The 3- bit counter counts clockwise and anti-clockwise direction based on an external input.

## Excitation tables

# Excitation table of D flip-flop: -

Qt	Q <sub>t+1</sub>	D
0	0	0
0	1	1
1	0	0
1	1	1

(Clk=1)

### For the 3-bit counter: -

Qt			Button	Q <sub>t+1</sub>			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
Q <sub>2</sub>	Q <sub>1</sub>	$\mathbf{Q}_{0}$	(B)	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	1	0	0
0	0	1	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0	0	0
0	1	0	0	Χ	X	X	Χ	Χ	Χ
0	1	0	1	X	X	X	X	Χ	Χ
0	1	1	0	1	1	1	1	1	1
0	1	1	1	0	1	0	0	1	0
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	0	1	1	0	1
1	0	1	0	Χ	Χ	Χ	Χ	Χ	Χ
1	0	1	1	Χ	X	X	Χ	Χ	Χ
1	1	0	0	0	0	1	0	0	1
1	1	0	1	1	1	1	1	1	1
1	1	1	0	1	0	1	1	0	1
1	1	1	1	1	1	0	1	1	0

ullet K-maps & simplified Boolean expressions for  $D_0$ ,  $D_1$ ,  $D_2$ 

 $D_2 = Q_1B' + Q'_0B$ 

$Q_2Q_1$						
Q <sub>0</sub> B		00	01	11	10	
	00	0	X	1	0	
	01	1	Х	1	1	
	11	0	0	0	Х	
	10	0	1	1	Х	

 $D_1 = Q_2B + Q_0B'$ 

$\mathrm{Q}_2\mathrm{Q}_1$						
Q <sub>0</sub> B		00	01	11	10	
	00	0	Х	0	0	
	01	0	Х	1	1	
	11	0	0	1	Х	
	10	1	1	1	Х	

 $D_0 = Q_1B + Q'_2B'$ 

$\mathrm{Q}_2\mathrm{Q}_1$						
Q <sub>0</sub> B		00	01	11	10	
	00	1	Х	0	0	
	01	0	Х	1	0	
	11	0	1	1	Х	
	10	1	1	0	Х	


### 2. D flip-flop

• Design source file

```
-- Company:
-- Engineer: DE SILVA A D D T
-- Create Date: 03/07/2024 11:56:08 AM
-- Design Name:
-- Module Name: D_FF - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity D FF is
    Port ( D : in STD_LOGIC;
           Res : in STD LOGIC;
           Clk : in STD_LOGIC;
           Q : out STD_LOGIC;
           Qbar : out STD_LOGIC);
end D_FF;
architecture Behavioral of D_FF is
begin
   process (Clk) begin
        if (rising_edge(Clk)) then
            if Res = '1' then
                Q <= '0';
                Qbar <= '1';
```

```
else
      Q <= D;
      Qbar <= not D;
      end if;
    end if;
    end process;
end Behavioral</pre>
```

• Elaborated design schematic

 


• Simulation source file

```
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity D_FF_Sim is
-- Port ( );
end D_FF_Sim;
architecture Behavioral of D_FF_Sim is
component D FF is
    Port ( D : in STD_LOGIC;
           Res : in STD_LOGIC;
           Clk : in STD_LOGIC;
           Q : out STD_LOGIC;
           Qbar : out STD_LOGIC);
end component;
signal D, Res, Q, Qbar : STD_LOGIC;
signal Clk : STD_LOGIC := '0';
begin
UUT : D_FF
    PORT MAP(
       D=>D,
        Res=>Res,
        Clk=>Clk,
        Q=>Q,
        Qbar=>Qbar);
```

```
PROCESS
BEGIN
    Clk<=NOT(Clk);</pre>
    WAIT FOR 20 NS;
END PROCESS;
PROCESS
BEGIN
    Res<='1';
    D<='0';
    WAIT FOR 50 NS;
    Res<='0';
    D<='0';
    WAIT FOR 50 NS;
    D<='1';
    WAIT FOR 50 NS;
    D<='0';
    WAIT FOR 50 NS;
END PROCESS;
end Behavioral;
```

• Timing diagram

 

#### 3. Slow clock

• Design source file


```
-- Company:
-- Engineer:
-- Create Date: 03/07/2024 12:39:32 PM
-- Design Name:
-- Module Name: Slow_Clk - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;
architecture Behavioral of Slow_Clk is
signal count : integer := 1;
signal clk status : std logic := '0';
```

```
begin

process (Clk_in) begin
   if (rising_edge(Clk_in)) then
        count <= count+1;
   if(count= 5) then
        clk_status <= not clk_status;
        Clk_out <= clk_status;
        count <= 1;
        end if;
   end process;

end Behavioral;</pre>
```

• Elaborated design schematic

 

• Simulation source file

```
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Slow Clk Sim is
-- Port ();
end Slow_Clk_Sim;
architecture Behavioral of Slow_Clk_Sim is
component Slow_Clk
    port (Clk_in : in std_logic;
          Clk_out : out std_logic);
end component;
signal Clk in : std logic :='0';
signal Clk_out : std_logic;
begin
UUT : Slow_Clk
    port map (
        Clk_in=>Clk_in,
        Clk_out=>Clk_out);
process
    begin
        Clk_in<= not Clk_in;</pre>
        wait for 20 ns;
end process;
end Behavioral;
```

Timing diagram



#### 4. Counter


• Design source file

```
- Company:
 - Engineer: DE SILVA A D D T
-- Create Date: 03/07/2024 01:35:50 PM
-- Design Name:
-- Module Name: Counter - Behavioral
-- Project Name:
-- Target Devices:
 - Tool Versions:
-- Description:
 - Dependencies:
-- Revision:
 -- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
 - arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
```

```
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Counter is
    Port ( Dir : in STD_LOGIC;
           Res : in STD LOGIC;
           Clk : in STD_LOGIC;
           Q : out STD_LOGIC_VECTOR (2 downto 0));
end Counter;
architecture Behavioral of Counter is
component D FF is
    Port ( D : in STD_LOGIC;
           Res : in STD_LOGIC;
           Clk : in STD_LOGIC;
           Q : out STD_LOGIC;
           Qbar : out STD_LOGIC);
end component;
component Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end component;
-- add your signal declarations here
signal D0,D1,D2:std logic;
signal Q0,Q1,Q2:std_logic;
signal Clk_slow:std_logic;
begin
Slow_Clk0:Slow_clk
   port map(
   Clk_in=>Clk,
   Clk_out=>Clk_slow
    );
D_FF0 : D_FF
PORT MAP(
     D=>D0,
     Res=>Res,
```

```
Clk=>Clk_slow,
     Q=>Q0
    );
D_FF1 : D_FF
PORT MAP(
     D=>D1,
     Res=>Res,
     Clk=>Clk_slow,
     Q=>Q1
);
D_FF2 : D_FF
PORT MAP(
     D=>D2,
     Res=>Res,
     Clk=>Clk_slow,
     Q=>Q2
    );
D0<=((not Q2) and (not Dir)) or (Q1 and Dir);
D1<=(Q2 and Dir) or (Q0 and (not Dir));
D2 < = (Q1 \text{ and (not Dir)}) \text{ or (Dir and (not Q0))};
Q(0)<=Q0;
Q(1)<=Q1;
Q(2)<=Q2;
end Behavioral;
```

• Elaborated design schematic

 

Simulation source file

```
- Company:
 - Engineer: DE SILVA A D D T
-- Create Date: 03/07/2024 01:42:01 PM
-- Design Name:
-- Module Name: Counter_sim - Behavioral
-- Project Name:
-- Target Devices:
 - Tool Versions:
 - Description:
 - Dependencies:
-- Revision:
 - Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
```


```
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Counter_sim is
-- Port ();
end Counter_sim;
architecture Behavioral of Counter sim is
component Counter is
    Port ( Dir : in STD LOGIC;
           Res : in STD_LOGIC;
           Clk : in STD_LOGIC;
           Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;
signal Dir, Res: std_logic;
signal Q : std_logic_vector(2 downto 0);
signal Clk : std_logic:='0';
begin
UUT : Counter
    port map(
    Clk => Clk,
    Dir=>Dir,
    Res=>Res,
    Q=>Q);
process
    begin
        Clk <= not Clk;</pre>
        wait for 5 ns;
end process;
process
begin
    Res <= '1';
    wait for 100 ns;
    Res <= '0';
```

```
Dir <= '0';
  wait for 700 ns;


Res <= '0';
  Dir <= '1';
  wait for 700 ns;
end process;

end Behavioral;</pre>
```


### • Timing diagram

 

• Implemented design schematic

 

#### Constraints file

 

#### 5. Conclusion

In this lab we used D flip-flops to design the counter. But we can also use JK flip-flops to design the counter. We used 'Dir' switch to change the direction of the counter. We can verify the functionality of the circuit via simulation and on the development board.